

---

# **Fit for Wireless**

## **Prepare yourself for RF-challenges**

### **Some basics (excerpt)**

Dr.-Ing. Gerald Oberschmidt

Ingenieurbüro ibdriGO

Hofäckerstraße 9, 76707 Hambrücken, Germany

Mail: [go@ibdrigo.com](mailto:go@ibdrigo.com)

Transmission Lines

Practical Transmission Lines

Passives


# Introduction to Transmission Line Theory

# Two-Port Parameters of Lines I

Transmission Lines

Practical Transmission Lines

Passives

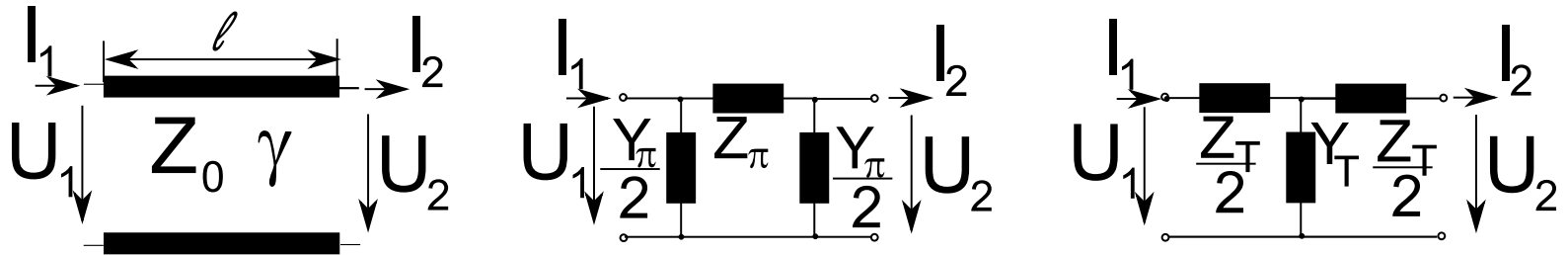

Transmission line and T- and  $\Pi$ -equivalent circuit

- A transmission line is (abstractly) nothing else than a symmetrical two-port
- All symmetrical two-ports can be expressed as T- or  $\Pi$ -equivalent circuits. Possibly (or rather certainly) the elements are strongly frequency dependent!

# Two-Port Parameters of Lines II

Transmission Lines

Practical Transmission Lines

Passives

- The  $\Pi$ -ckt has equations

$$U_2 = U_1 \left( 1 + \frac{1}{2} Z_\pi Y_\pi \right) + Z_\pi I_1$$

$$I_2 = I_1 \left( 1 + \frac{1}{2} Z_\pi Y_\pi \right) + U_1 Y_\pi \left( 1 + \frac{1}{4} Z_\pi Y_\pi \right)$$

- At the same time the line-equations in mathematical form are

$$U_2 = U_1 \cosh \gamma l + Z_0 I_1 \sinh \gamma l$$

$$I_2 = I_1 \cosh \gamma l + \frac{U_1}{Z_0} \sinh \gamma l$$

- Finally we find (summarized for both eq.ckt.)

$$Z_\pi = Z_0 \sinh \gamma l \quad Y_\pi = \frac{2}{Z_0} \tanh \frac{\gamma l}{2}$$

$$Y_T = \frac{1}{Z_0} \sinh \gamma l \quad T_T = 2Z_0 \tanh \frac{\gamma l}{2}$$

# Electrically Short Transmission Lines

The above derived equivalent circuits are especially interesting for short transmission lines (i.e.  $\gamma l \ll \lambda$ )

In that case the hyperbolic functions are approximated as  $\sinh \gamma l \approx \gamma l$ ,  $\cosh \gamma l \approx 1$ ,  $\tanh \frac{\gamma l}{2} \approx \frac{\gamma l}{2}$

And so we obtain  $Z_\pi \approx Z_0 \gamma l \approx j\omega \sqrt{\epsilon_r \epsilon_0 \mu_0} Z_0 l$  which looks very much like an inductance, and  $Y_\pi \approx \gamma l / Z_0 \approx j\omega \sqrt{\epsilon_r \epsilon_0 \mu_0} / Z_0 l$  which looks like a capacitance.

Which is dominant is mostly dependent on  $Z_0$ . For large  $Z_0$  there is a dominant series inductance with small (parasitic) shunt capacitance. For a small  $Z_0$  we see capacitive behavior with parasitic inductance.

Similar here are the parameters of the T-equivalent circuit:  $Y_T \approx 1/Z_0 \sinh \gamma l \approx j\omega \sqrt{\epsilon_r \epsilon_0 \mu_0} Z_0$ , again, this is a capacitance and also  $Z_T \approx Z_0 \gamma l \approx j\omega \sqrt{\epsilon_r \epsilon_0 \mu_0} / Z_0$ . The latter is now the missing (evtl. parasitic) inductance.

These figures are much used in design of low-pass filters as we will see later.

# Micro-Strip-Line

Transmission Lines

Practical Transmission Lines

● Micro-Strip-Line


● Micro-Strip: COUPLED

LINES


● Coupling

Passives

## Geometry

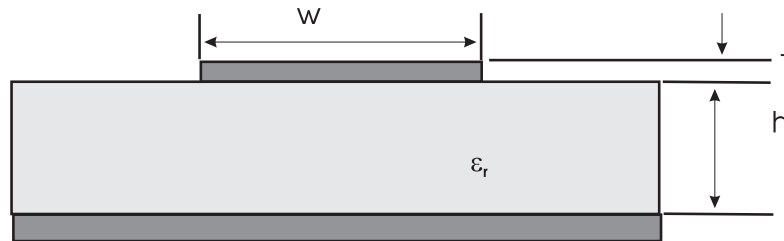

## Impedance and effective permittivity

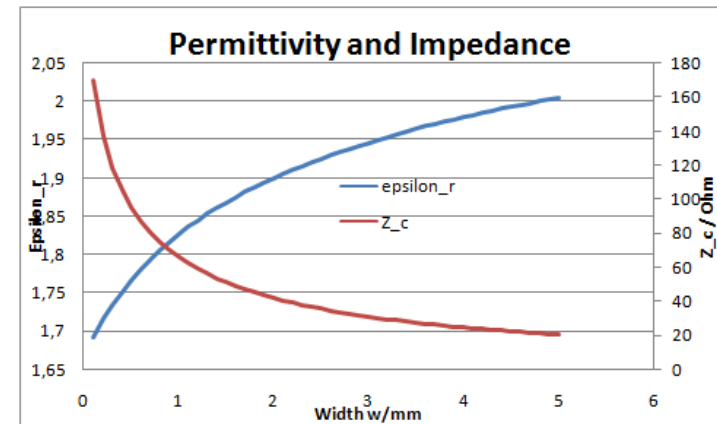

( $\epsilon_r = 2.2$   $h = 0.5$  mm)

# Micro-Strip Line: Some Remarks

Transmission Lines

Practical Transmission Lines

● Micro-Strip-Line

● Micro-Strip: COUPLED

LINES

● Coupling

Passives

- Relatively easy to handle in PCB
- OPEN is OK, but not perfect (to be seen later)
- SHORT only manufacture-able with via (not ideal, either)
- BENDS/ CURVES should be mitered
- (Quasi-static) Effective design formulas exist, also for buried or multi-layered micro-strip lines
- Watch out for
  - ◆ Disturbances in Ground plane
  - ◆ Coupling to other lines
  - ◆ Disturbances (e.g. shielding cages) in vicinity of the line!
  - ◆ substrate may be an-isotropic, i.e.  $\epsilon_r$  differs with direction.

# Calculation of Effective Properties of MS

Effective dielectric constant:

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \sqrt{1 + \frac{12H}{W}}^{-1} + F(\epsilon_r, H) - 0.217(\epsilon_r - 1) \frac{T}{\sqrt{WH}}$$

with

$$F(\epsilon_r, H) = \begin{cases} 0.02(\epsilon_r - 1)(1 - W/H)^2, & \text{for } W/H < 1 \\ 0 & \text{for } W/H > 1 \end{cases}$$

Die characteristic impedance is

$$Z_c = \sqrt{\frac{\epsilon_0 \mu_0}{\epsilon_{eff}}} \frac{1}{C_a}$$

with

$$C_a = \begin{cases} \frac{2\pi\epsilon_0}{\ln(8H/W + 4W/H)} & W/H \leq 1 \\ \epsilon_0 [W/H + 1.393 + 0.667 \ln(W/H + 1.444)] & W/H > 1 \end{cases}$$



# Micro-Strip: OPEN

Transmission Lines

Practical Transmission Lines

● Micro-Strip-Line

● Micro-Strip: COUPLED

LINES

● Coupling

Passives



(real) open



$dl$  effective add length



Eff. add cap

- Micro-strip open end is effectively described by length extension or
- Effective capacitance at end of the line
- The wider the strip is, the longer is the effective extension

# Micro-Strip: SHORT/ VIA

Transmission Lines

Practical Transmission Lines


● Micro-Strip-Line

● Micro-Strip: COUPLED

LINES

● Coupling

Passives

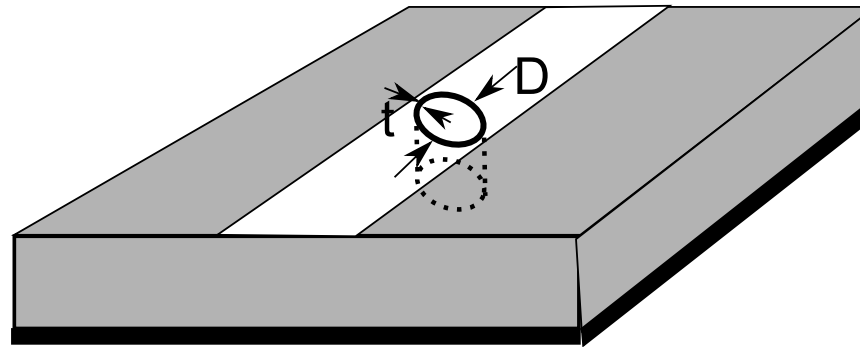

MS via of diameter  $D$  and thickness  $t$

- Micro-strip via is described by series resistance and inductor to ground
- Series resistance: Depends on DC res. of structure (i.e. specific resistance of material) and on skin-effect (current only at outer boundary of via)
- Inductance is dominant

# Micro-Strip: BENDS

Transmission Lines

Practical Transmission Lines


● Micro-Strip-Line

● Micro-Strip: COUPLED


LINES

● Coupling


Passives

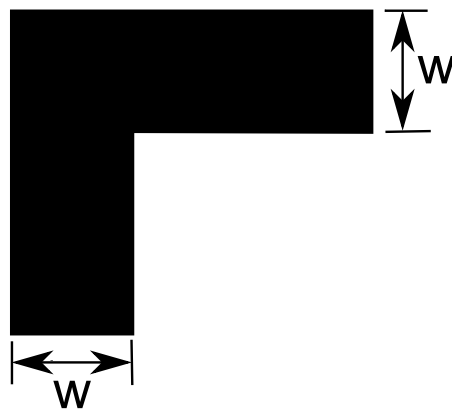

90° bend

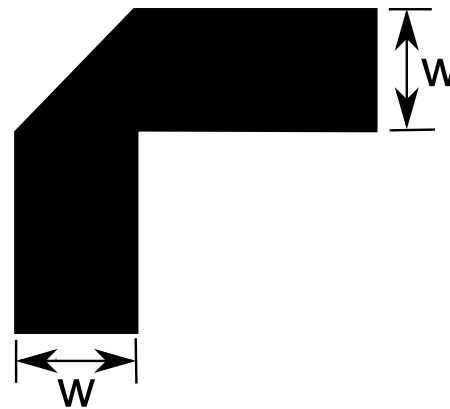

50% mitered bend

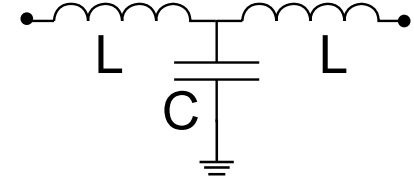

T equivalent circuit

- Micro-strip bend should be conducted as mitered bends
- Miter acts as “Mirror” so that the wave “sees” the line going on straight
- Equivalent circuit is a T-diagram with L and C

# Micro-Strip: COUPLED LINES

Transmission Lines


Practical Transmission Lines

● Micro-Strip-Line

● Micro-Strip: COUPLED LINES

● Coupling

Passives

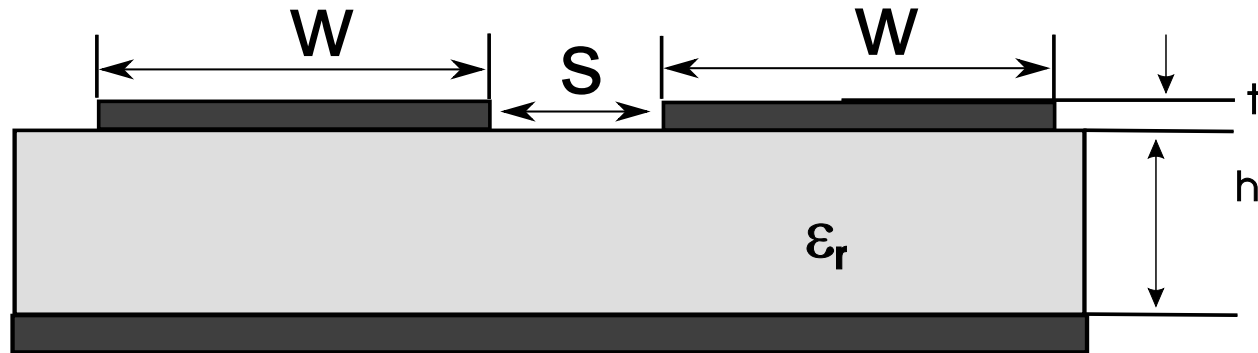

- Supports two modes: Even and Odd thus supports two different impedances:  $Z_o, Z_e$ .
- Coupling between lines  $C = \frac{Z_e - Z_o}{Z_e + Z_o}$
- Characteristic impedance of line-system is geometric mean of even and odd mode  $Z_0 = \sqrt{Z_e Z_o}$
- Usage in coupler structures!
- Unwanted parasitics: Two micro-strip lines in parallel are couplers, thus: Do not get too close

# Micro-Strip: Coupled Lines


Transmission Lines

Practical Transmission Lines

● Micro-Strip-Line  
● Micro-Strip: COUPLED  
LINES

● Coupling

Passives

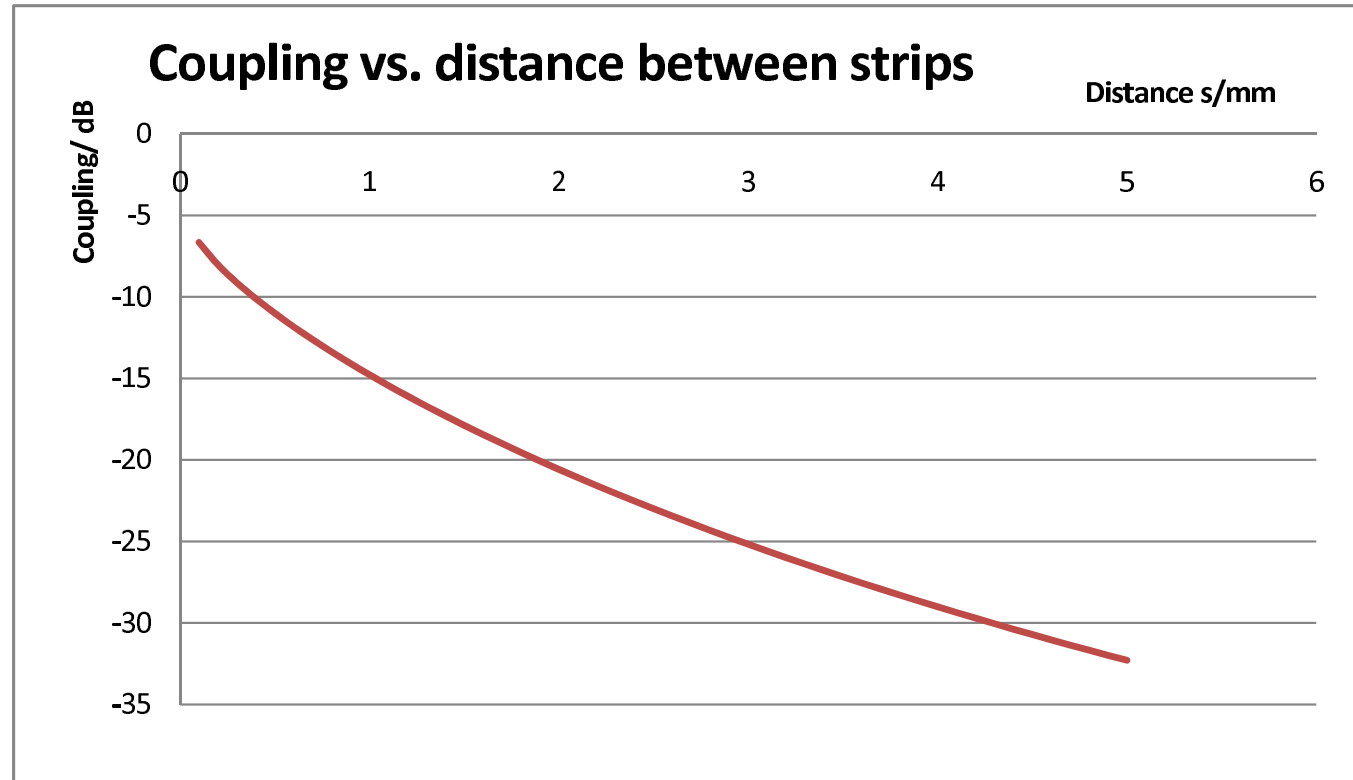

Micro-strip couples lines ( $w = 1\text{mm}$ ,  $h = 1\text{mm}$ ,  $\epsilon_r = 9.7$ )  
Coupling for even  $2w$  spacing between the lines is still significant!

# Stripline

Transmission Lines


Practical Transmission Lines

● Micro-Strip-Line

● Micro-Strip: COUPLED LINES

● Coupling

Passives

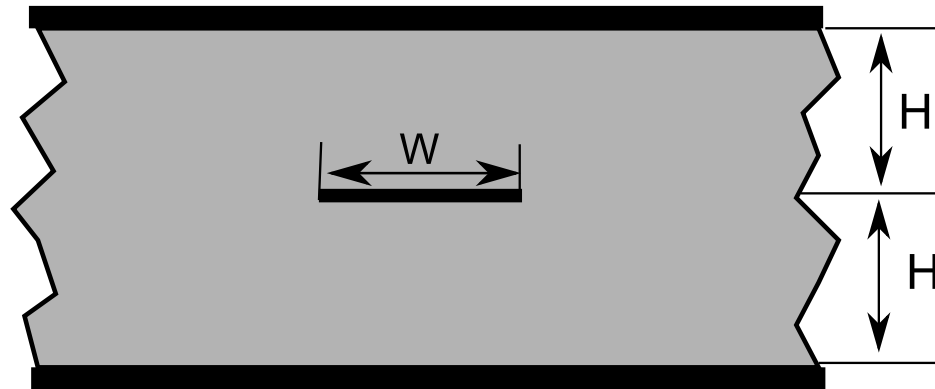

- Shielded to both: top and bottom
- Can be almost fully shielded when vias are used at sides
- Electrical field better confined due to higher effective permittivity ( $\epsilon_{eff} = \epsilon_r$ ), low dispersion
- Requires at least three layers

# Stripline: Coupled

Transmission Lines


Practical Transmission Lines

● Micro-Strip-Line

● Micro-Strip: COUPLED LINES

● Coupling

Passives

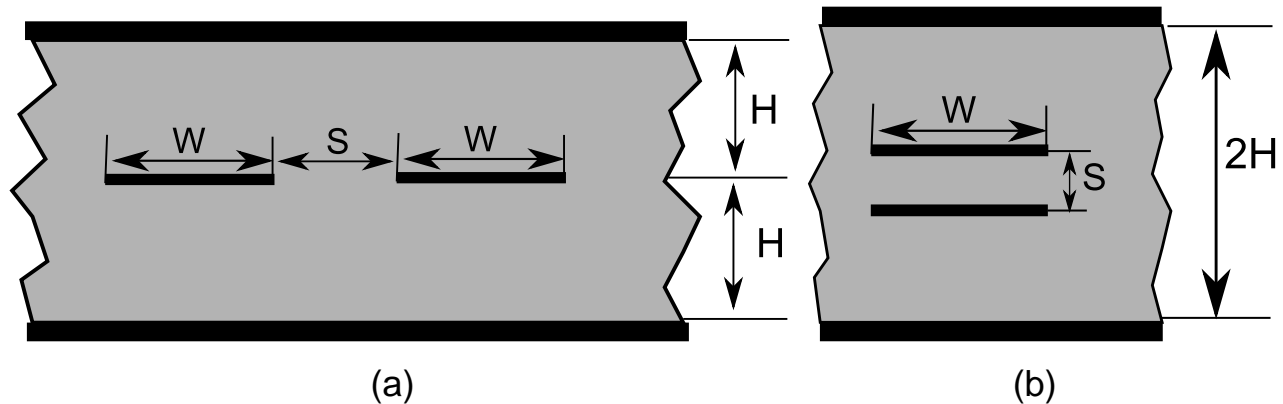

(a) Coplanar (a) and broadside (b) coupled striplines

- Coplanar: All in one layer
- Broadside: Lines in different layers

# Coupling of Practical Lines


Transmission Lines

Practical Transmission Lines

● Micro-Strip-Line  
● Micro-Strip: COUPLED  
LINES

● Coupling

Passives

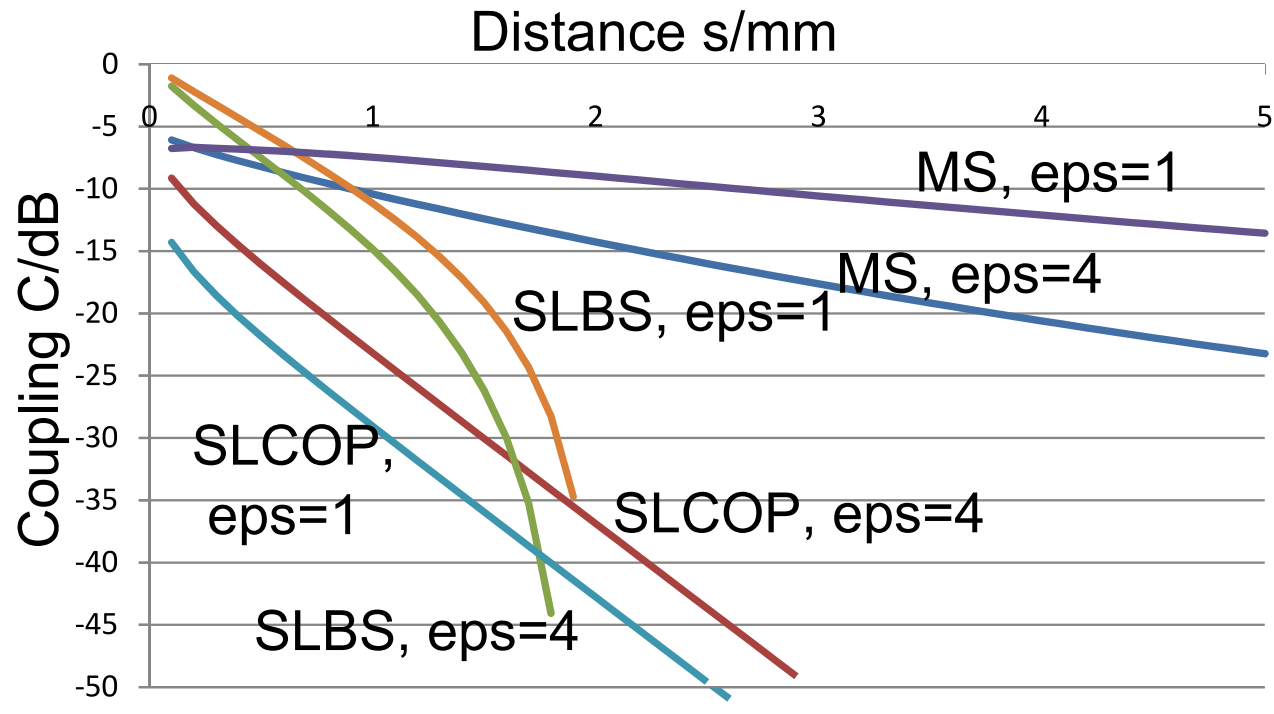

- Micro-strip line has highest coupling, Coplanar coupled stripline best de-coupling

Parameters:  $h = 1 \text{ mm}$ ,  $Z_0 = 50 \Omega$  for (centered) strip,  $\Rightarrow$

Name	Short	$(w/mm, \epsilon_r = 1)$	$(w/mm, \epsilon_r = 1)$
Strip, broadside	SLBS	2.9	1.0
Strip, coplanar	SLCOP	2.9	1.0
Micro-strip	MS	5.0	2.1



Transmission Lines


Practical Transmission Lines

**Passives**

- Attenuator
- Filter Design

# Passive Components and Filters

# Simple Resistive Attenuators

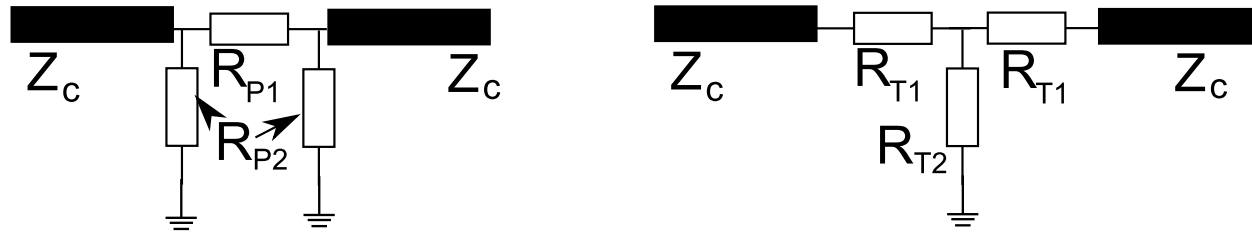

For an attenuation ratio  $c = u_2/u_1$  the resistors are to be dimensioned as (equal characteristic impedances  $Z_c$  at both sides)

- T-circuit  $R_{T1} = \frac{1-c}{1+c} Z_c$ ,  $R_{T2} = \frac{2c}{1-c^2} Z_c$
- $\Pi$ -circuit calculated from T-model via star-triangular transform:  $R_{P1} = R_{T1} \frac{2R_{T1} + R_{T2}}{R_{T2}}$ ,  $R_{P2} = R_{T1} + 2R_{T2}$
- Note: There is power to be absorbed in the attenuator, thus thermal issues may occur!
- See next slide for example values

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

# Attenuator: Resistive Values

Resistor values for attenuators at  $Z_c = 50\Omega$

Att./ dB	$U_1/U_2$ (lin)	$R_{P1}/\Omega$	$R_{P2}/\Omega$	$R_{T1}/\Omega$	$R_{T2}/\Omega$
0.25	0.97	1.4	3474.6	0.7	1736.9
0.5	0.94	2.9	1737.7	1.4	868.1
1	0.89	5.8	869.5	2.9	433.3
2	0.79	11.6	436.2	5.7	215.2
3	0.71	17.6	292.4	8.5	141.9
5	0.56	30.4	178.5	14.0	82.2
10	0.32	71.2	96.2	26.0	35.1
20	0.10	247.5	61.1	40.9	10.1
30	0.03	789.8	53.3	46.9	3.2

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

# Filter Design

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

Filter needed for

- RF-RX: RF selection (reject blockers, limit bandwidth, thus minimize noise bandwidth)
- RF-TX: Keep spectrum clean, do not disturb others! Shape spectrum.
- IF: Separate wanted and unwanted signal (e.g. LO rejection), reject image frequencies

Filter development

- Systematic approach to design frequency response
- Translate from prototype (low-pass) filters wanted shape (e.g. bandpass)
- Translate into physical structures. Here: transmission-lines

# Prototype-Filters

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design


■ Starting point: Power-Loss-Ratio  $P_{LR} = \frac{1}{1-\rho^2} = \frac{1}{1-|\Gamma|^2}$

■ Express with well defined ratio of polynomials:

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

■ Butterworth-filter for  $N(\omega^2) = 1$  and  $M(\omega^2) = k^2(\omega/\omega_c)^{2N}$

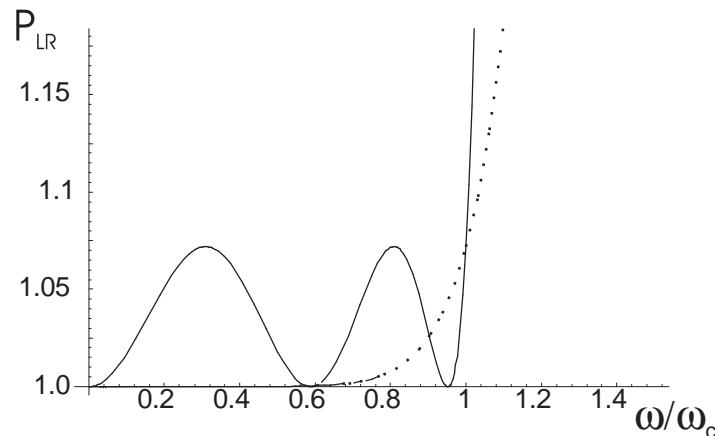■ Chebycheff-filter for  $N(\omega^2) = 1$  and  $M(\omega^2) = k^2 T_N^2(\omega/\omega_c)$  for Chebycheff-characteristic.  $T_N$ : Chebycheff-Polynomial order  $N$



Characteristics for  
Butterworth- (- - -) und  
Chebycheff-low-pass (—)  
order 5

# Prototype Filter Characteristics



Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

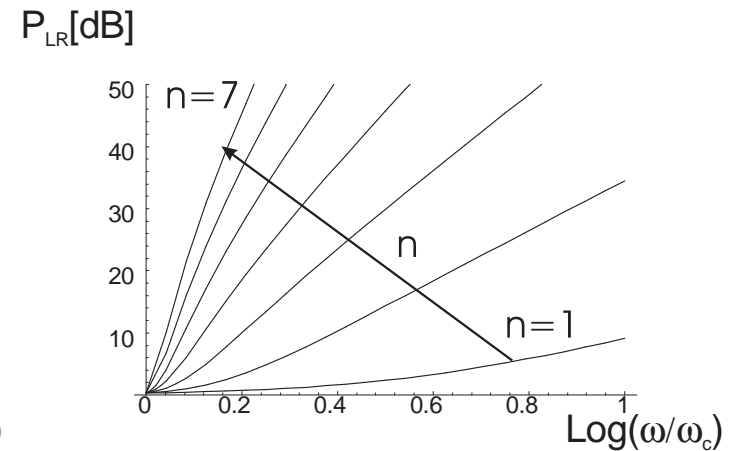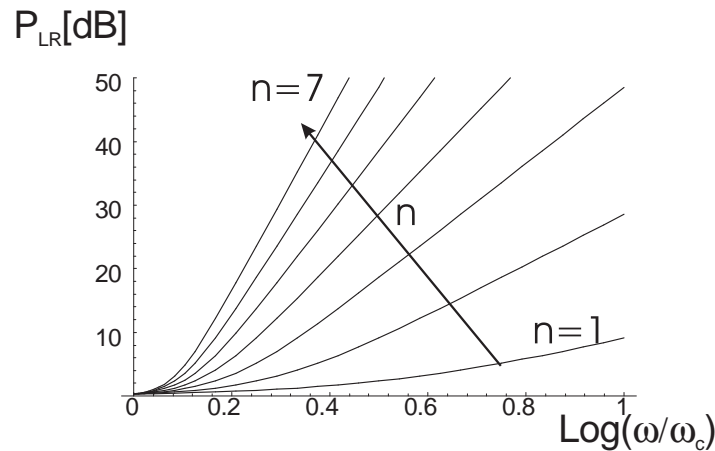

(a) (b)  
Rejection-characteristics for different order filters ripple  
 $\rho_{max} = 1$  dB. (a) Butterworth, (b) Chebycheff.

- Chebycheff:
  - ◆ Highest possible (polynomial) selection
  - ◆ Ripples in pass-band
- Butterworth:
  - ◆ Maximum flat in passband
  - ◆ Fairly low rejection

# Filter Prototype Structure


Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

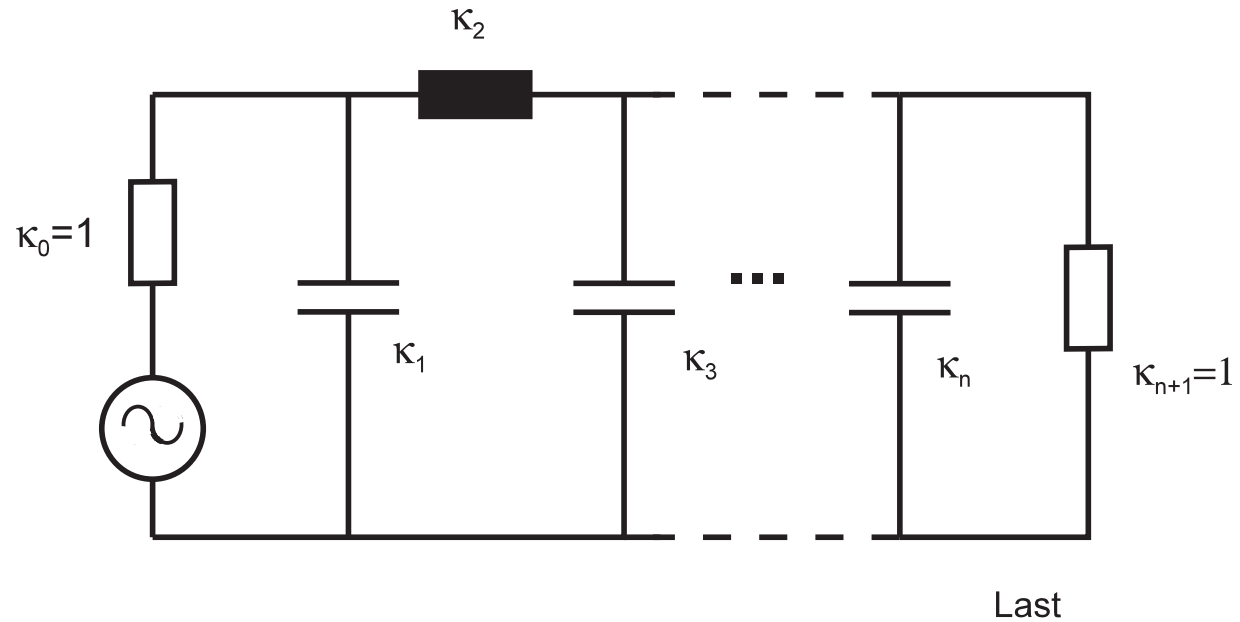

Low-pass prototype, starting with cap.

# Element Values: Butterworth

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

n	1	2	3	4	5	6	7
$\kappa_1$	2	1.4142	1	0.7654	0.6180	0.5176	0.4450
$\kappa_2$	1	1.4142	2	1.8478	1.6180	1.4142	1.2470
$\kappa_3$		1	1	1.8478	2	1.9319	1.8019
$\kappa_4$			1	0.7654	1.6180	1.9319	2
$\kappa_5$				1	0.6180	1.4142	1.8019
$\kappa_6$					1	0.5176	1.2470
$\kappa_7$						1	0.4450
$\kappa_8$							1

Prototype Elements for Butterworth filter

- All orders terminate in 1  $\Rightarrow$  All orders lead to matched filter
- Elements calculated with  $L_k = \frac{\kappa_k Z_0}{\omega}$  and  $C_k = \frac{\kappa_k}{\omega Z_0}$
- $\omega$  is 3 dB corner frequency,  $Z_0$  impedance level (here: 50  $\Omega$ )



# Element Values: Chebycheff

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

n	1	2	3	4	5	6	7
$\kappa_1$	1.018	1.822	2.024	2.099	2.135	2.155	2.166
$\kappa_2$	1	0.685	0.994	1.064	1.091	1.104	1.112
$\kappa_3$		2.660	2.024	2.831	3.001	3.063	3.093
$\kappa_4$			1	0.789	1.091	1.152	1.174
$\kappa_5$				2.660	2.135	2.937	3.093
$\kappa_6$					1	0.810	1.112
$\kappa_7$						2.660	2.166
$\kappa_8$							1

Table of prototype values for Chebycheff low-pass with  
 $\rho_{max} = 1 \text{ dB}$

- Only odd orders terminate in 1, thus only they can be matched to  $50 \Omega$

# Recipe for Low-Pass-Filter

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

1. Select corner frequencies  $\omega$ , maximum loss (ripple)  $\rho_{max}$  in pass-band, selectivity
2. Selection of maximum ripple determines which table (from elaborate literature) to use. Standard values for  $\rho_{max}$  are usually tabulated
3. Selectivity requirements determine order. Evtl. use graphics for this
4. Take prototype (normalized) values  $\kappa_n$
5. Carry values over to physical network with  $L_k = \frac{\kappa_k Z_0}{\omega}$  and  $C_k = \frac{\kappa_k}{\omega Z_0}$
6. If transmission line-design wanted, use formulae for short lines and calculate length  $l_L = \frac{\lambda_L}{2\pi} \arcsin(\omega C Z_L)$  for low impedance ( $L$ ) and  $l_H = \frac{\lambda_H}{2\pi} \arcsin\left(\frac{\omega L}{Z_H}\right)$  for high impedance ( $H$ ) section.

# Example: Low-Pass in Micro-strip Technology

## Design requirements

- Butterworth, order  $\geq 5$  (we will chose 7)
- Low-pass up to 1 GHz, high rejection for  $f \approx 10$  GHz
- Design for  $50 \Omega$  in microstrip-technology, on RT-Duroid 5880,  $\epsilon_r = 2.2$ ,  $h=0.508$  mm
- Chose impedances (should be manufacturable, only supporting one mode and still as far apart as possible),  
 $Z_H = 120 \Omega$ ,  $w_H = 0.27$  mm;  
 $Z_L = 15 \Omega$ ,  $w_L = 7.3$  mm
- Compensation done empirically (just scale length of lines)

Element	Value	el. l uncomp.	phys.l/mm comp.
$C_1$	1.4 pF	$7.7^\circ$	3.6
$L_1$	9.9 nH	$31^\circ$	16.4
$C_2$	5.7 pF	$33^\circ$	15.6
$L_2$	16 nH	$56^\circ$	29.6
$C_3$	5.7 pF	$33^\circ$	15.6
$L_3$	9.9 nH	$31^\circ$	16.6
$C_4$	1.4 pF	$7.7^\circ$	3.6

# Low-pass-Filter Layout


Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

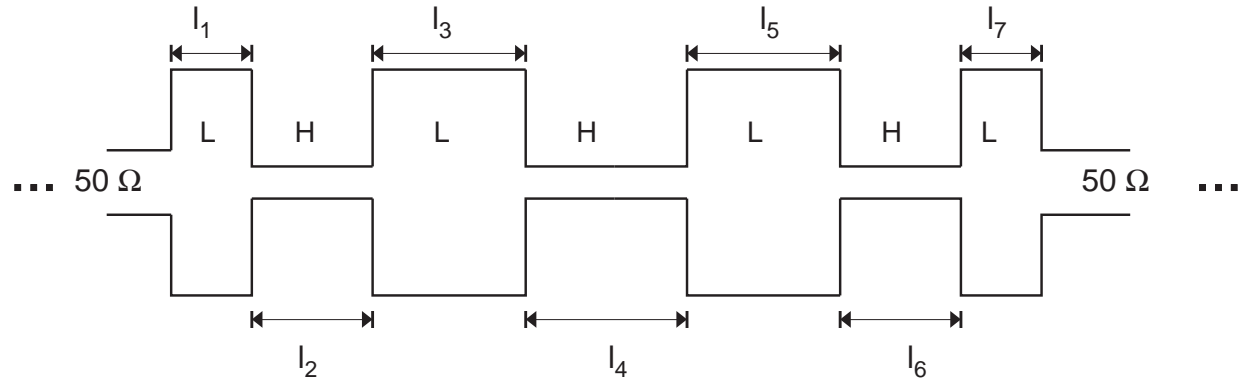

Micro-strip-layout of a Butterworth low-pass.

# Low-Pass-results

Transmission Lines

Practical Transmission Lines

Passives



● Attenuator

● Filter Design

09 Dec 2008

Ansoft Corporation  
XY Plot 2  
Circuit1

13:11:12

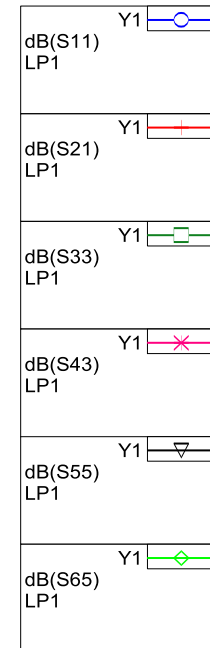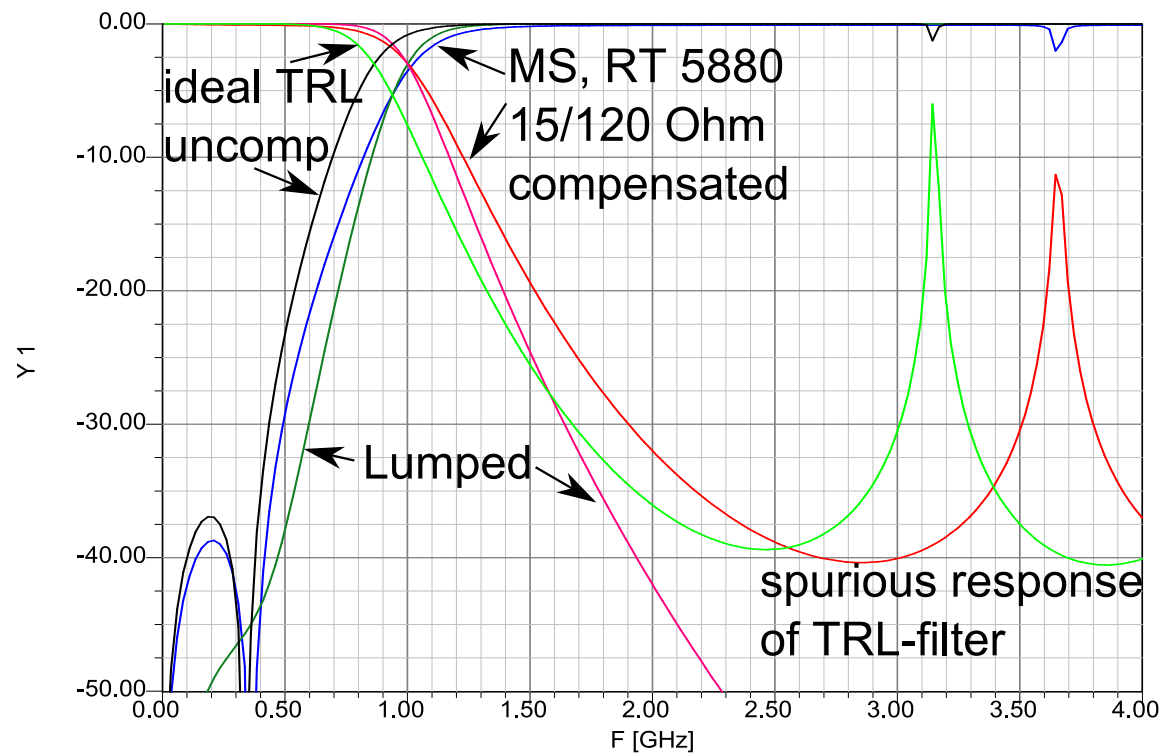

# Design of Distributed Band-Pass-Filter

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

- General approach is to transform prototype low-pass to band via a transformation function (for band-pass:

$$b(\omega) = \frac{\omega_0}{\Delta\omega} \left( \frac{\omega_0}{\omega} - \frac{\omega}{\omega_0} \right)$$

- Bandpass with coupled line section design equations:

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\Theta_1 = \frac{\pi \omega_1}{2\omega_0},$$

$$P \sin \Theta_1 = \frac{K'_{10}}{\sqrt{\frac{1}{2} \tan \Theta_1 + K'_{10}{}^2}},$$

$$s = \frac{1}{\frac{1}{2} \tan \Theta_1 + K'_{10}{}^2}.$$

# Design of Distributed Band-Pass-Filter

Transmission Lines

Practical Transmission Lines

Passives

● Attenuator

● Filter Design

- Values for impedance normalized (to  $Z_c$ ) impedance inverters:

$$K'_{10} = K'_{n+1,n} = \frac{1}{\sqrt{\kappa_0 \kappa_1}} = \frac{1}{\sqrt{\kappa_n \kappa_{n+1}}} ,$$

$$K'_{k,k+1} = \frac{1}{\sqrt{\kappa_k \kappa_{k+1}}} .$$

- Some values come to aid:

$$\hat{N}_{k+1,k} = \sqrt{K'^2_{k+1,k} + \frac{1}{4} \tan^2 \Theta_1}$$

- And finally the even- and odd-mode impedances

$$Z_e^1 = Z_e^{n+1} = Z_c(1 + P \sin \Theta_1) ,$$

$$Z_o^1 = Z_o^{n+1} = Z_c(1 - P \sin \Theta_1) ,$$

$$Z_e^{k+1} = Z_e^{n-k+1} = Z_c S(\hat{N}_{k+1,k} + K'_{k+1,k}) ,$$


$$Z_o^{k+1} = Z_o^{n-k+1} = Z_c S(\hat{N}_{k+1,k} - K'_{k+1,k}) .$$

# Design Results for Bandpass

Chebyscheff, 1 dB equal-ripple filter, pass-band 11 ... 12 GHz, on 50  $\Omega$ -System, Order  $N = 7$  Impedances in  $\Omega$ , Symmetry

$$Z_{N-k} = Z_k$$

$Z_{e1}$	62.0	$Z_{o1}$	37.9
$Z_{e2}$	51.3	$Z_{o2}$	43.2
$Z_{e3}$	50.6	$Z_{o3}$	43.8
$Z_{e4}$	50.5	$Z_{o4}$	43.9

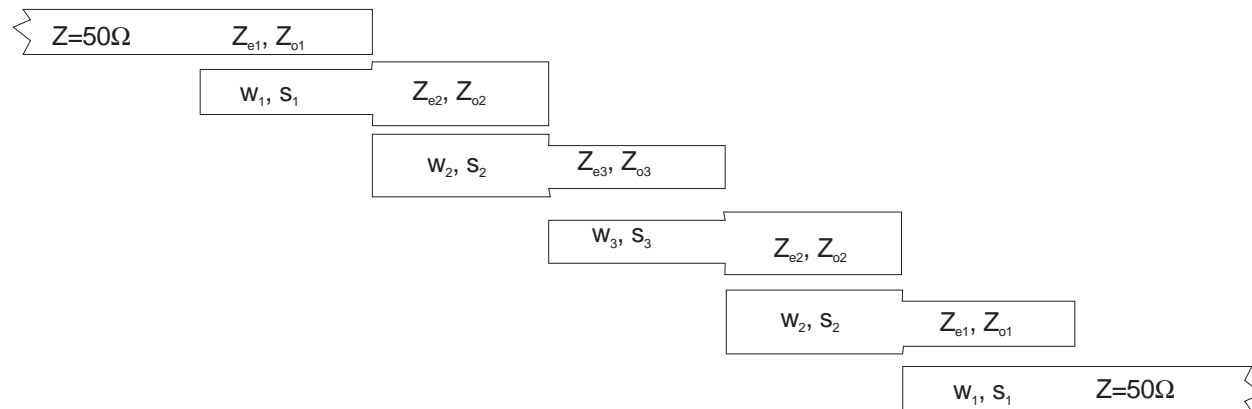

Layout (schematically) of a bandpass filter in microstrip technology





# Bandpass Results I

09 Dec 2008

Ansoft Corporation  
XY Plot 1  
Circuit1

14:39:38

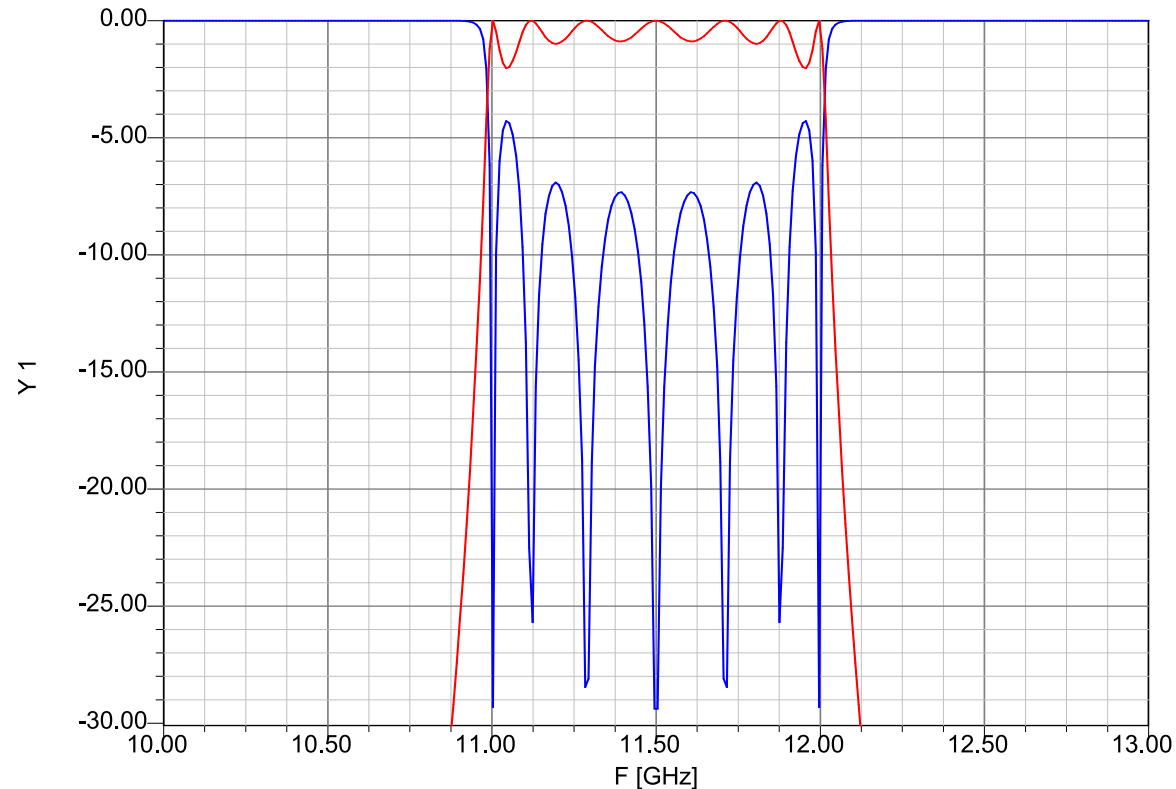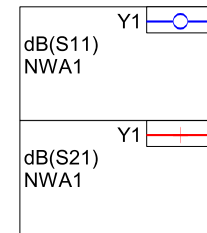



Simulation for bandpass filter (N=7) with ideal coupled transmission-lines (no end-effect, no real lines considered). Observe the number of ripples!

# Bandpass Results II

09 Dec 2008

Ansoft Corporation  
XY Plot 1  
Circuit1

14:41:16

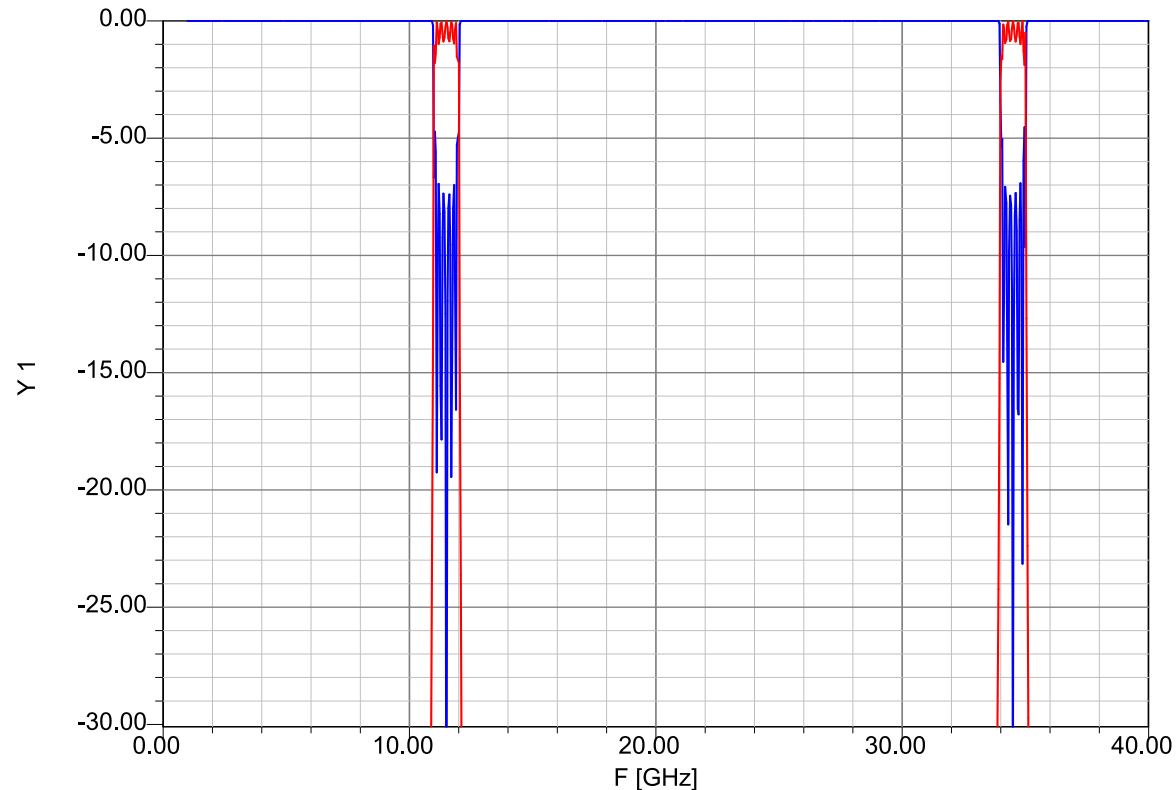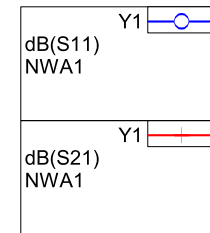

Simulation as above, observe the spurious pass-band at  $3f_0$ , where the lines have an electrical length of  $3\lambda/2$ . No passband at length  $\lambda$ !